

ASSIGNMENT

Sai Kiran
saikiran30407@gmail.com

FWC22146

IIT Hyderabad-Future Wireless Communication

Contents

1 Problem	2
2 Components	2
3 Reduction of logical circuit	2
4 Implementation	3
5 Procedure	4

1 Problem

Q.35. If $X = X_1X_0$ and $Y = Y_1Y_0$ are 2-bit binary numbers. The Boolean function S that satisfies the condition "If $X > Y$, then $S = 1$ ", in its minimized form, is ?

1. $X_1Y_1 + X_0Y_0$
2. $X_1\overline{Y_1} + X_0\overline{Y_0}Y_1 + X_0\overline{Y_0}X_1$
3. $X_1\overline{Y_1}X_0\overline{Y_0}$
4. $X_1Y_1 + X_0\overline{Y_0}Y_1 + X_0\overline{Y_0}X_1$

2 Components

Component	Values	Quantity
ArduinoUNO		1
JumperWires	M-M	6
Breadboard		1
LED		5
Resistor	220ohms	5

3 Reduction of logical circuit

$$X = X_1X_0 \quad Y = Y_1Y_0$$

The boolean function S that satisfies the condition, if $X > Y$, then $S = 1$.

We can represent the above condition through a truth table.

X X_1X_0	Y Y_1Y_0	S $X>Y$
0 0	0 0	0
0 0	0 1	0
0 0	1 0	0
0 0	1 1	0
0 1	0 0	1
0 1	0 1	0
0 1	1 0	0
0 1	1 1	0
1 0	0 0	1
1 0	0 1	1
1 0	1 0	0
1 0	1 1	0
1 1	0 0	1
1 1	0 1	1
1 1	1 0	1
1 1	1 1	0

Table 1: TRUTH TABLE FOR $S = X>Y$

By using k-maps, we can find the boolean expression for the condition, $S = 1$ if, $X>Y$

		Y_1Y_0			
		00	01	11	10
X_1X_0	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

Minimized form: $S = X_1\overline{Y_1} + X_1X_0\overline{Y_0} + X_0\overline{Y_1}\overline{Y_0}$

4 Implementation

arduino		output
2	resistor	led 1 (X_1)
3	resistor	led 2 (X_0)
4	resistor	led 3 (Y_1)
5	resistor	led 4 (Y_0)
8	resistor	led 5 (S)

Table 2:

5 Procedure

1. Connect the circuit as per the above table.
2. The leds 1,2,3,4 represent the values of X_1, X_0, Y_1 and Y_0 respectively.
3. The led 5 represent S . if the condition $X > Y$ is true.
4. Execute the circuits using the below code.

<https://github.com/saikiran-1309/FWC/blob/main/in-gate-2019-35/code/src/comp.cpp>